

# Celebrating 100 years of Amateur Radio in Tasmania - 2023 (If you wanted a transmitter 100 years ago, you had to build it!)

A project on behalf of NTARC.  
(The Northern Tasmanian Amateur Radio Club Inc.)

## UPDATE #1

**Diode – Reverse Polarity Protection**  
**RF CHOKE Note**  
**CRYSTAL OSCILLATOR Improvement**  
**MODIFICATIONS for 40m**  
**Adding SIDETONE**

### The Century “Cent” (1 Watt) 80m CW Transmitter Mk I


#### 1. REVERSE POLARITY PROTECTION

As a safeguard to connecting the power supply/ 12v battery the wrong way round, I added a silicon diode (mine is a 3A IN5408, but you can use anything similar.)
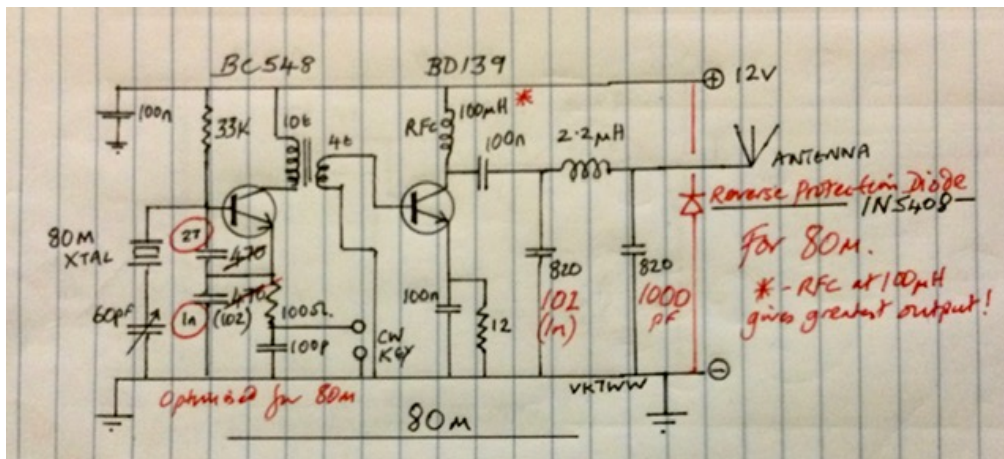
#### 2. RF CHOKE

It is recommended that a 100uH RFC be used.

Tests with various values of RFC (e.g. 30uH and below) reduced the RF Output considerably.




#### 3. CRYSTAL OSCILLATOR Improvement (80m)

After finding some old FT243, HC6U and 10X type quartz crystals for 80m, it was found that changing the two 470pf capacitors gave an improvement in output.

- The 470pf between the base and emitter change to 27pf.
- The 470pf to ground, change to 1n (102).

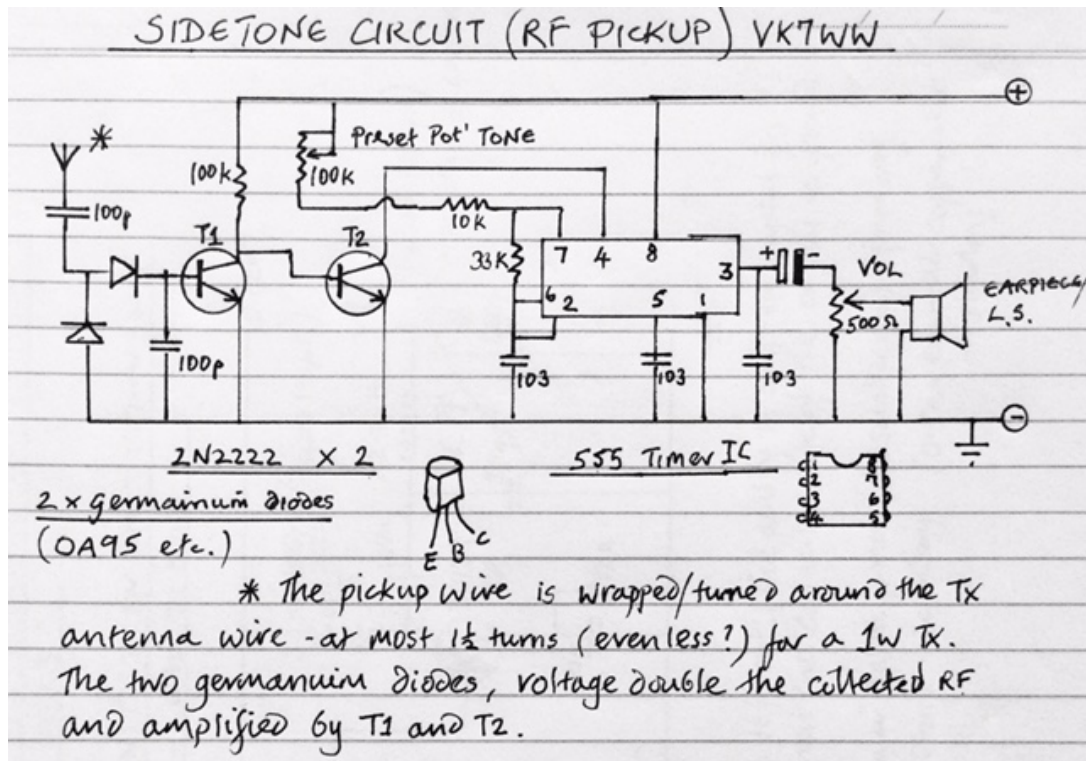(Trying a 40m xtal in the original, or modified circuit above, did not work successfully.)





The circuit picks up a small amount of RF, that is rectified through the two diodes acting as a voltage doubler. The two transistors further amplify the voltage before it is used to turn on the 555 timer IC, that acts as a tone oscillator. The tone is adjusted by the 100k pre-set pot', and the volume by the 500 ohm pot. A small loudspeaker or headphone insert can be used.


This can be built in a stand-alone box or fitted inside the Tx. One turn of the RF pickup wire, or less! ... is all that is needed for 1w or less. (See the WHITE Wire in the photo.) No loss in RF output was noted.


Two building methods are shown, the Island or Blob Board (Paddy Board) method and the "Criss-Cross" or "Zig-Zag" saw cut method.

Another "CENT" update soon: (Notes on using a DDS for the "CENT" and a real 80m VFO with Buffer). 73 Nic, VK7WW.


**See Photos Below:**



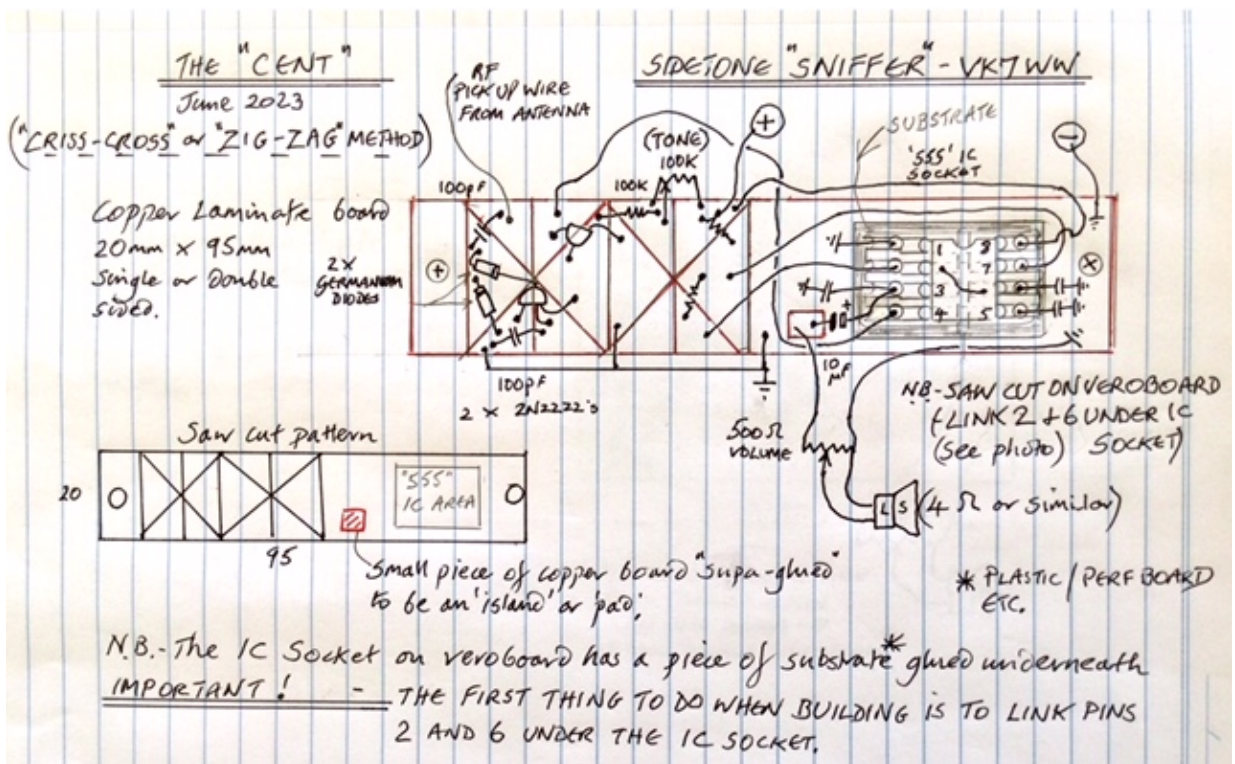

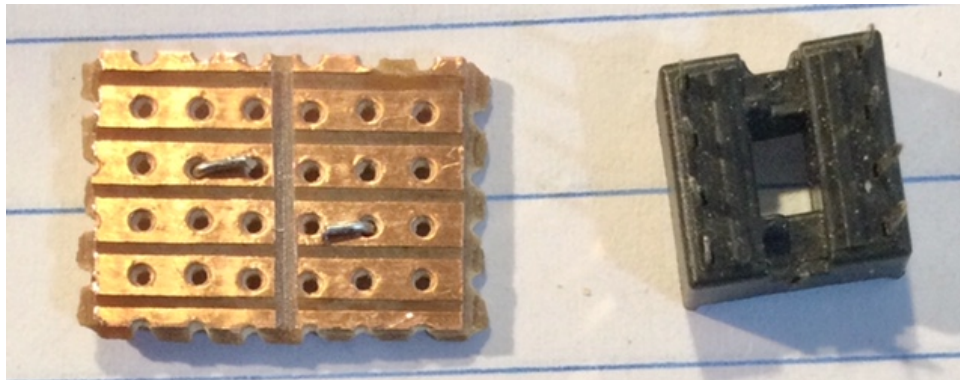


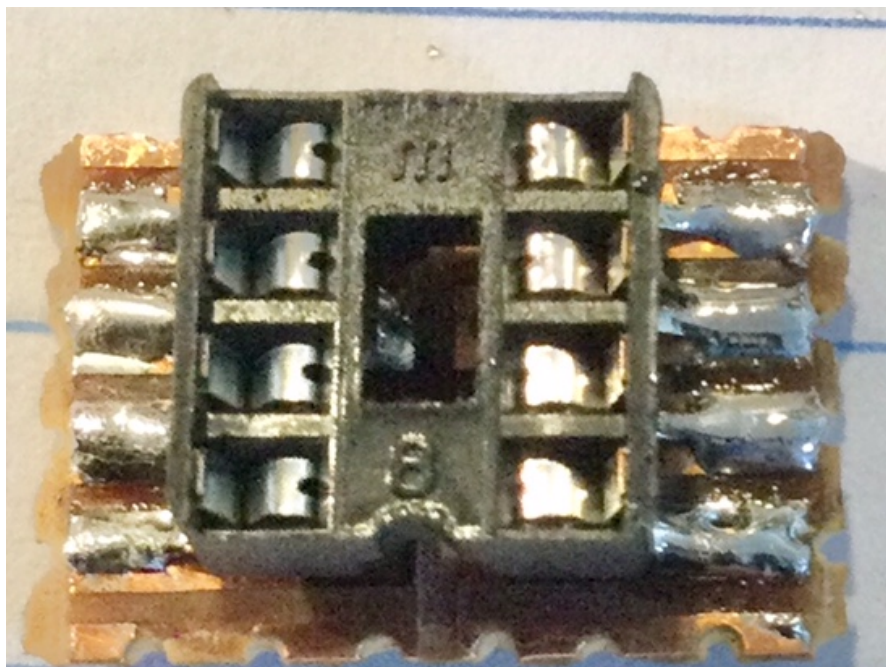IC socket soldered to copper side of veroboard  
Link between pins 2 & 6 in place for soldering



Note Saw-cut on Veroboard  
IC socket soldered in place  
(Assembly needs to be glued to substrate and then  
glued onto copper laminate board)

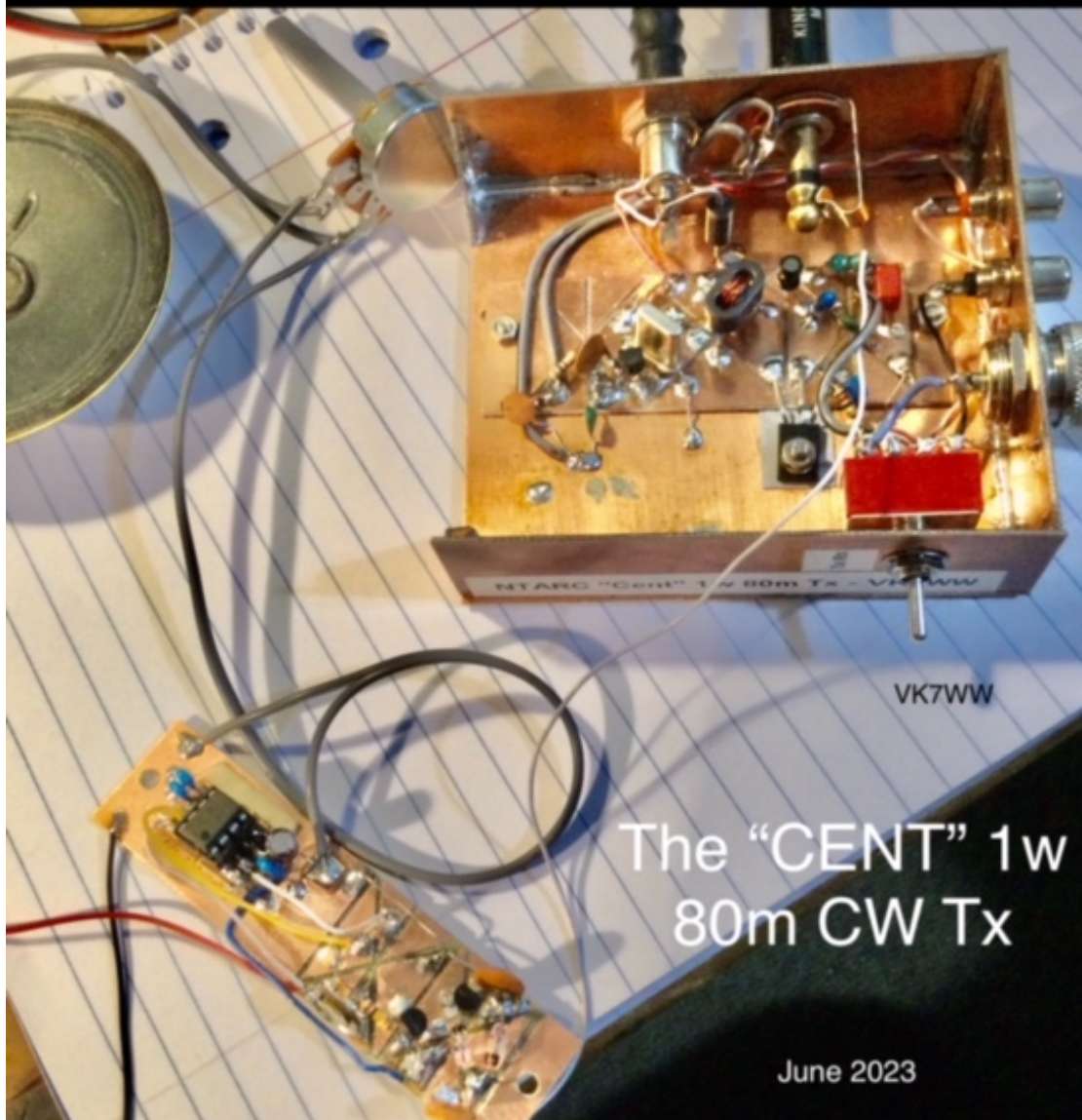Showing how little RF pickup is required for Sidetone (white wire next to grey antenna wire)



The "CENT" 1w  
80m CW Tx

June 2023